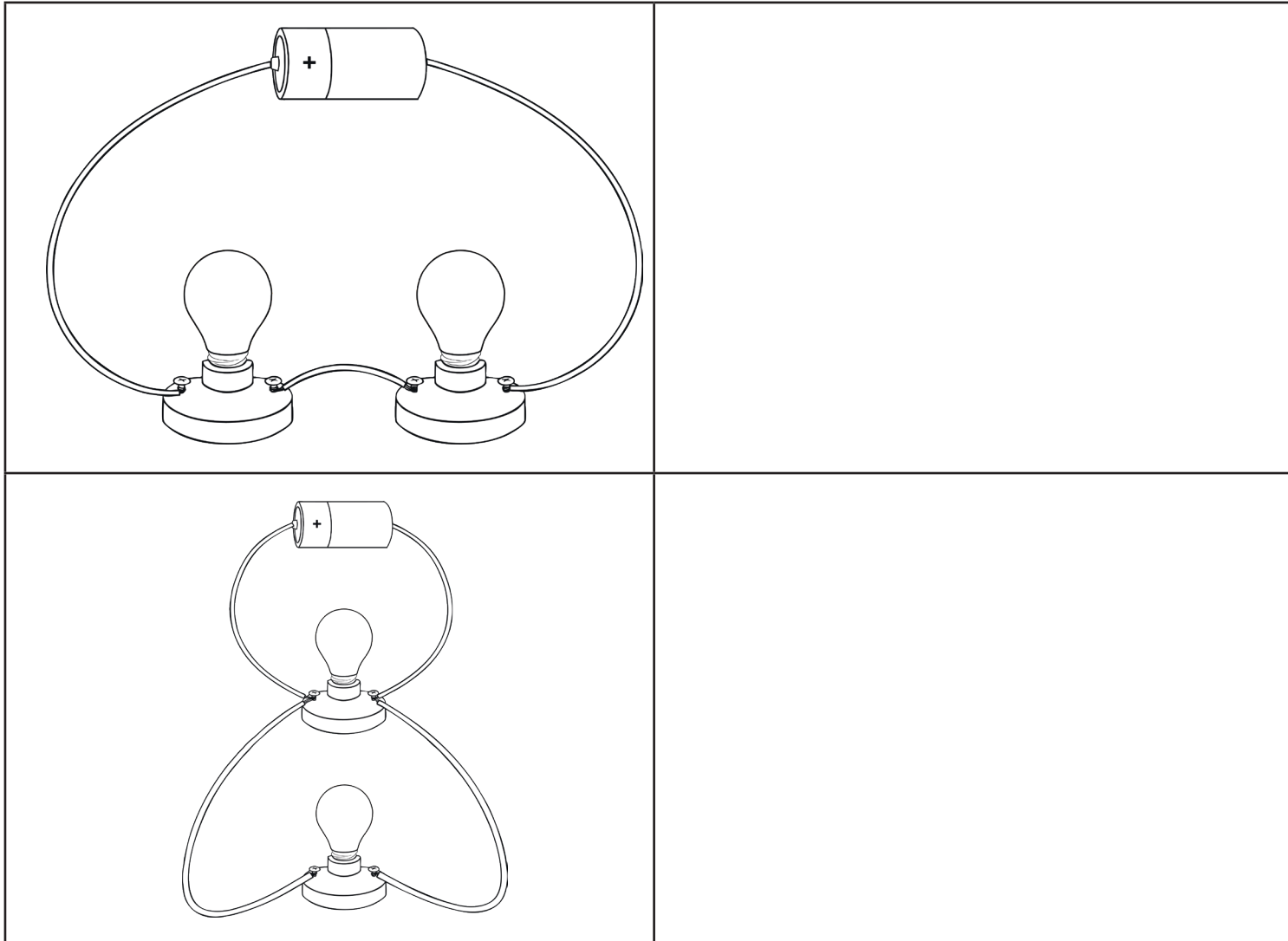


# Circuits


Make both of these circuits. Re-draw the series and parallel circuit using the symbols.



**lamp**




**motor**

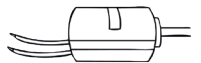

**battery**



**switch**

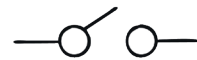

**buzzer**

